
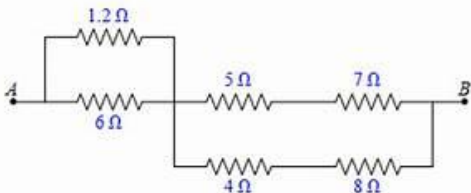


01 - Determine a resistência equivalente entre os pontos A e B.


I -

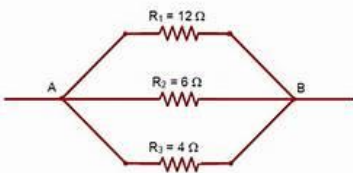


II -




III -

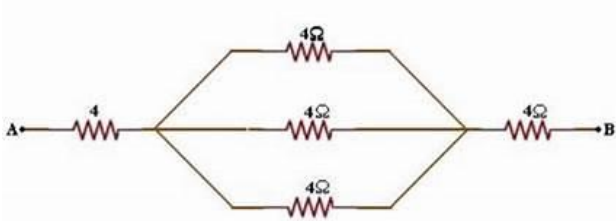


IV -

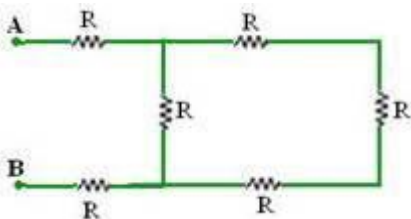


V -

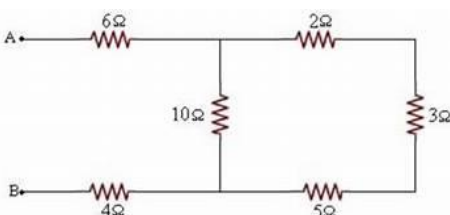


VI -

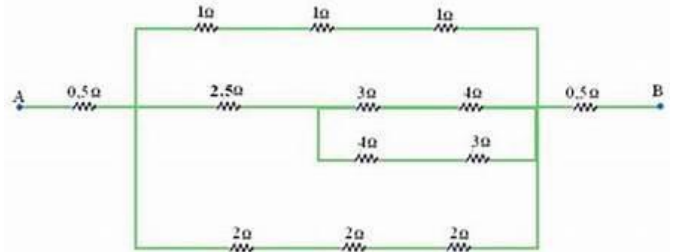

VII -

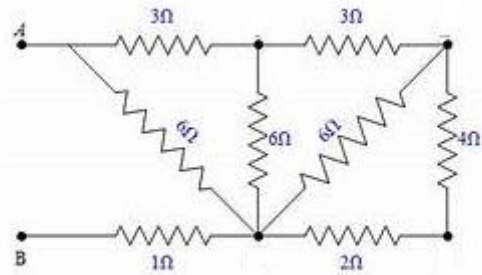

VIII -

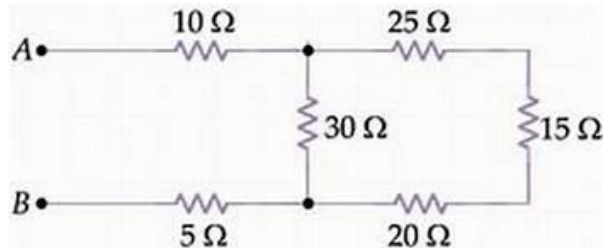

I - 7Ω II - 2Ω III - (28/3)Ω IV - (11/4)R V - 15Ω
 VI - 2,5Ω VII - 4Ω VIII - 35Ω